


Analog IC Design**Lab 10****Noise Simulation****Intended Learning Objectives**

In this lab you will:

- Learn how to simulate noise in a LPF in both ac and transient simulations.
- Learn how to simulate noise in a 5T OTA in both ac and transient simulations.

PART 1: LPF AC Noise Analysis

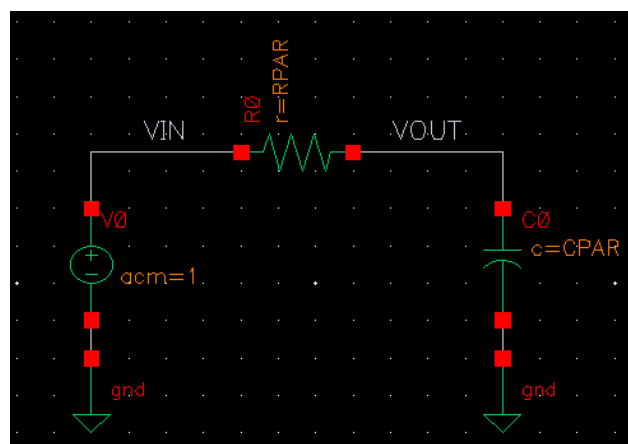- 1) Create a new cell “lab_09_noise_rc”. Create a testbench for a simple 1st order LPF as shown below. Set R and C as parameters.



- 2) Set up AC analysis (1Hz:10Gz, logarithmic, 10 points/decade).
- 3) Setup noise analysis as shown below.

Choosing Analyses -- ADE L (19)

Analysis: ☐ tran ☐ dc ☐ ac ☒ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☐ pz ☐ sp ☐ envlp ☐ pss
☐ pac ☐ pstb ☐ pnoise ☐ pxf
☐ psp ☐ qpss ☐ qpac ☐ qpnoise
☐ qpxf ☐ qpss ☐ hb ☐ hbac
☐ hbnoise ☐ hbss

Noise Analysis

Sweep Variable: ☒ Frequency
☐ Design Variable
☐ Temperature
☐ Component Parameter
☐ Model Parameter
☐ None

Sweep Range: ☒ Start-Stop Start: 1 Stop: 10G
☐ Center-Span


Sweep Type: ☒ Points Per Decade 10
☐ Number of Steps
 Add Specific Points ☐

Output Noise: ☒ voltage
 Positive Output Node: /VOUT
 Negative Output Node: /gnd!

Input Noise: ☒ voltage
 Input Voltage Source: /V0

Enabled ☒

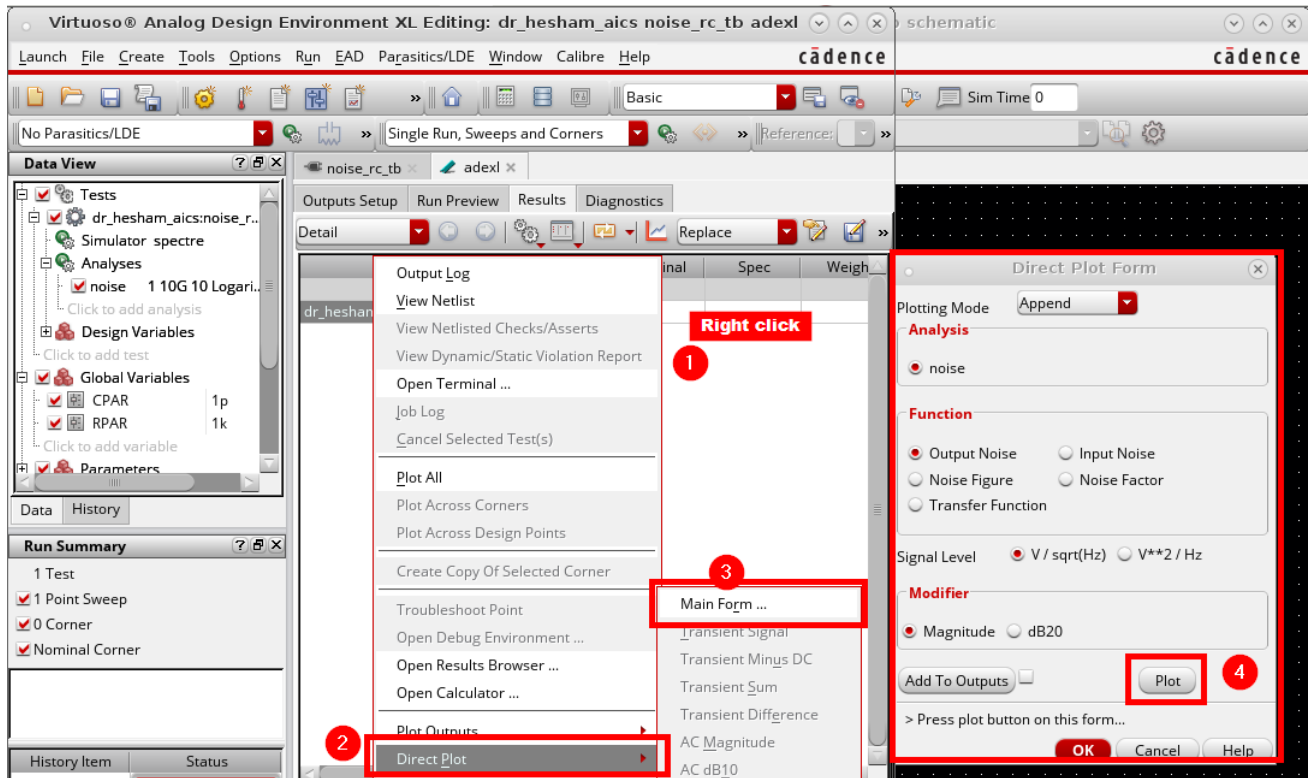- 4) Set RPAR = 1k and CPAR = 1p.
 - 5) Run noise analysis.
 - 6) Report output noise vs frequency. Annotate voltage noise density and bandwidth in the plot.
- ➔ Cadence Hint: From adexl Results tab, right click and choose "Direct Plot" -> "Main Form" as shown below.



7) Calculate rms output noise using rms noise function in the calculator.

➔ Cadence Hint: In the calculator use `rmsNoise(1 10G)`.

➔ Cadence Hint: Another very powerful tool for noise simulation is Noise Summary: From adexl Results tab, right click and choose "Print" -> "Noise Summary".

8) Compare the simulation results (noise density, bandwidth, and rms) with hand analysis.

9) Run parametric sweep for RPAR = 1k, 10k, 100k, 1000k.

10) Plot output noise overlaid on the same plot. Using log-scale for y-axis. Comment on the results.

11) Calculate the rms noise using the calculator. Comment on the results.

PART 2: LPF Transient Noise Analysis

1) Create a new simulation configuration for transient noise. Define new parameters TAU, TSTOP, and TSTEP as shown below.

Global Variables	
CPAR	1p
RPAR	1k
TAU	RPAR*CPAR
TSTOP	100*TAU
TSTEP	TAU/100

2) Setup transient noise analysis as shown below. Fmax is set to $1/TSTEP$ and Fmin is set to $1/TSTOP$. You can think of these as the start and end frequencies used in generating the noise samples (i.e., equivalent to the start and end frequencies used in integrating the PSD). Only one transient noise simulation run will be performed.

Choosing Analyses -- ADE L (19)

Analysis: ☒ tran ☐ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☐ pz ☐ sp ☐ envlp ☐ pss
☐ pac ☐ pstb ☐ pnoise ☐ pxf
☐ psp ☐ qpss ☐ qpac ☐ qpnoise
☐ qpxf ☐ qpss ☐ hb ☐ hbac
☐ hbnoise ☐ hbss

Transient Analysis

Stop Time: VAR("TSTOP")

Accuracy Defaults (errpreset): ☒ conservative ☐ moderate ☐ liberal

☒ Transient Noise

Noise Fmax: 1 / VAR("TSTEP")

Noise Fmin: 1 / VAR("TSTEP")

Noise Seed: 1

Noise Scale:

Noise Tmin: VAR("TSTEP")

Noise Update: ☒ step ☐ fmax

☐ Multiple Runs
Number of Runs: 100

Noise Contribution: ☐ on ☐ off

Instance List: [Select] [Clear]

Dynamic Parameter: ☐

Enabled: ☒ [Options...]

[OK] [Cancel] [Defaults] [Apply] [Help]

- 3) Report the noise output waveform. Annotate the min and max values.
- 4) Use the rms function in the calculator to calculate the rms noise. Compare it to the value calculated in Part 1.
- Cadence Hint: `rms(VT("/VOUT"))`
- 5) Repeat the simulation with $TSTEP = \tau/10$. Does the calculated rms noise increase or decrease? Why?
- 6) Back to $TSTEP = \tau/100$. Change the transient noise options as shown below. Now it will run 20 runs of transient noise iterations.

☒ Multiple Runs
Number of Runs: 20

- 7) Report the rms noise vs iteration.
- Cadence Hint: `rms(VT("/VOUT"))`
- 8) Use the calculator to calculate the average rms noise. Compare the calculated value with the rms noise previously obtained in Part 1 and Part 2.

PART 3: 5T OTA AC Noise Analysis

- 1) Create a new testbench. Connect the 5T OTA you designed in Lab 07 in unity-gain buffer configuration. Similar to Part 1, run ac noise analysis.
- 2) Report output thermal noise vs frequency. Annotate noise density and bandwidth in the plot. Compare the simulation results with hand analysis.
- 3) Report total output noise (thermal + flicker) vs frequency. Estimate the Flicker noise corner.
- 4) Calculate rms output noise (calculate the rms noise due to thermal noise only using Noise Summary).
- 5) Compare the simulation results (noise density, bandwidth, and rms) with hand analysis.

PART 4: 5T OTA Transient Noise Analysis

- 1) Create a new simulation configuration. Keep the 5T OTA connected in unity-gain buffer configuration.
- 2) Set the input signal as a sin wave with amplitude = 10mV and $f_{in} = 10\text{kHz}$ frequency superimposed on a CM level equal to the middle value of the CMIR.
- 3) Run transient analysis with max time step = $0.02/f_{in}$ (50 points for cycle) and stop time = $4/f_{in}$ (simulate 4 cycles).
- 4) Plot input and output overlaid and make sure they match well (verify that the circuit behaves as a buffer).
- 5) Now we will run transient noise analysis similar to Part 2. Use a single noise simulation run. Set transient noise upper frequency at 10 times the OTA GBW.
- 6) Report the “noisy” output waveform (zoom-in to highlight the noise). Notice that output signal and noise are superimposed.
- 7) Change the transient noise options to run 20 simulation runs. Now Spectre will run 20 runs of transient noise.
- 8) Report the rms noise vs iteration.
- 9) Use the calculator to calculate the average rms noise. Compare the calculated value with the rms noise previously obtained in Part 3.

Lab Summary

- In Part 1 you learned:
 - How to do ac noise simulation of a LPF.
 - How the rms noise change with the filter’s resistor value.
- In Part 2 you learned:
 - How to do transient noise simulation of a LPF.
 - The need for multiple transient simulation runs for plotting rms noise spectrum.
- In Part 3 you learned:
 - How to do ac noise simulation of a 5T OTA.
- In Part 4 you learned:

- How to do transient noise simulation of a 5T OTA.
- The need for multiple transient simulation runs for plotting rms noise spectrum.

Acknowledgements

Thanks to all who contributed to these labs. Special thanks to Dr. Sameh A. Ibrahim for reviewing and editing the labs. If you find any errors or have suggestions concerning these labs, contact Hesham.omran@eng.asu.edu.eg.