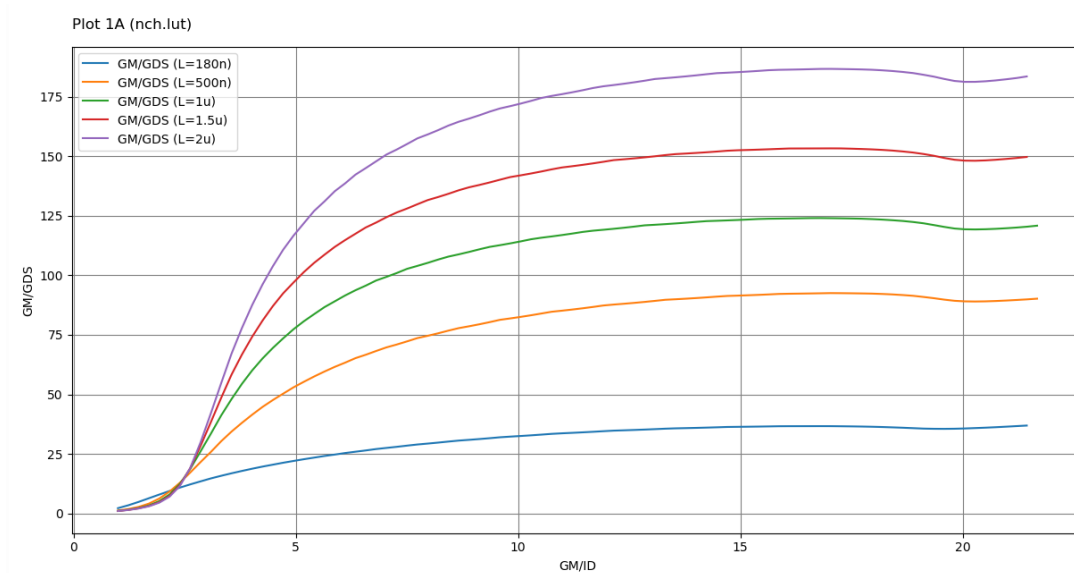


# Lab 11


## PART 1: gm/ID Design Charts

gm/gds

NMOS




PMOS

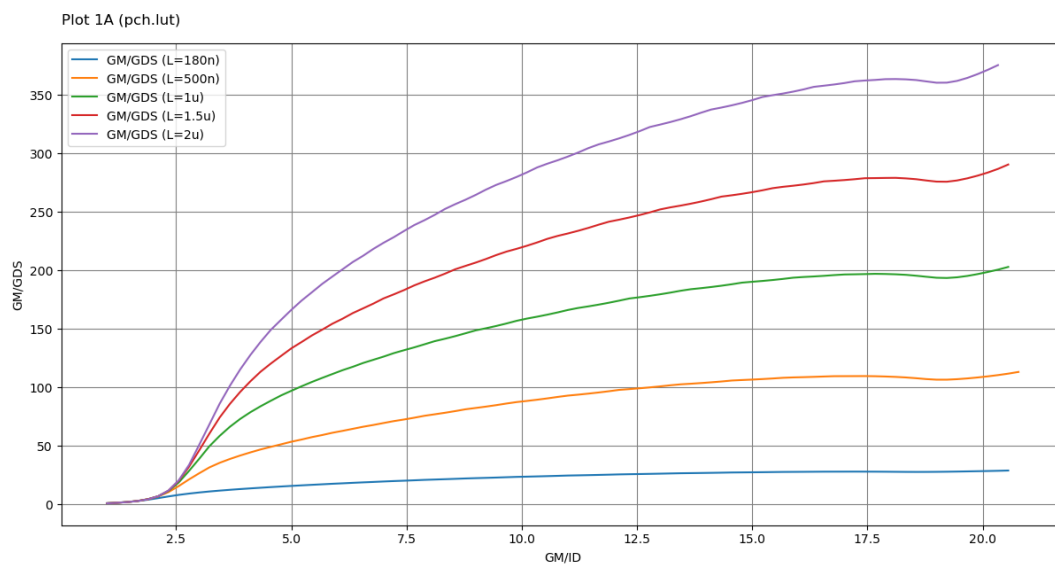


## ID/W

### NMOS

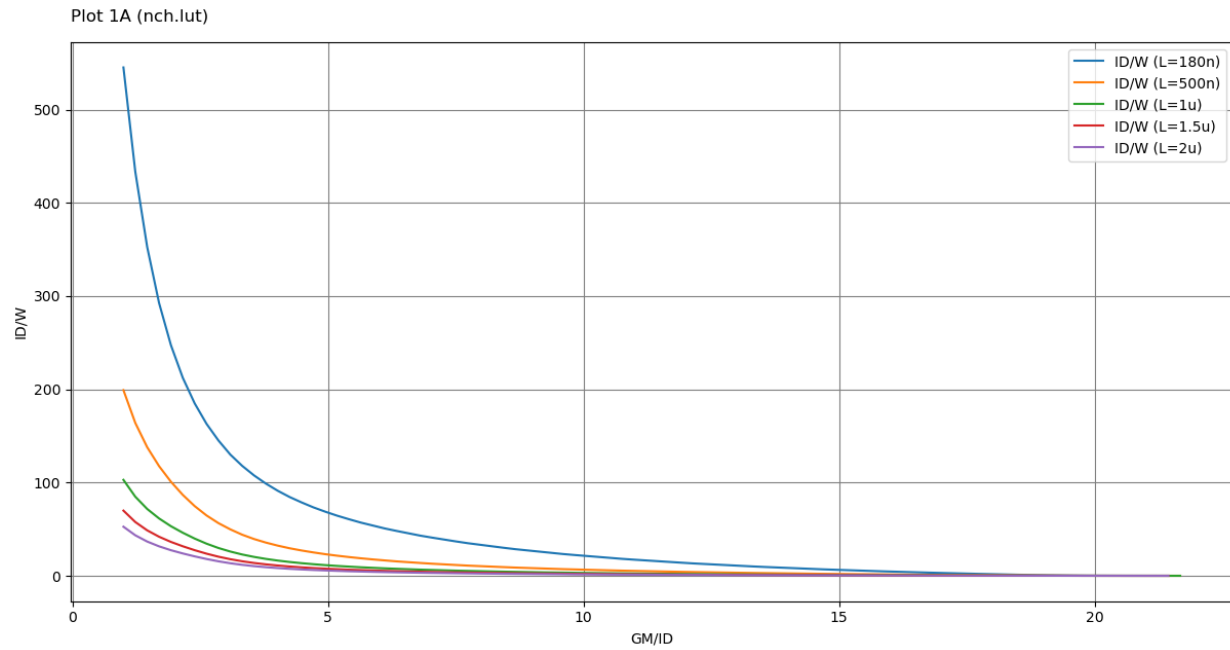


### PMOS

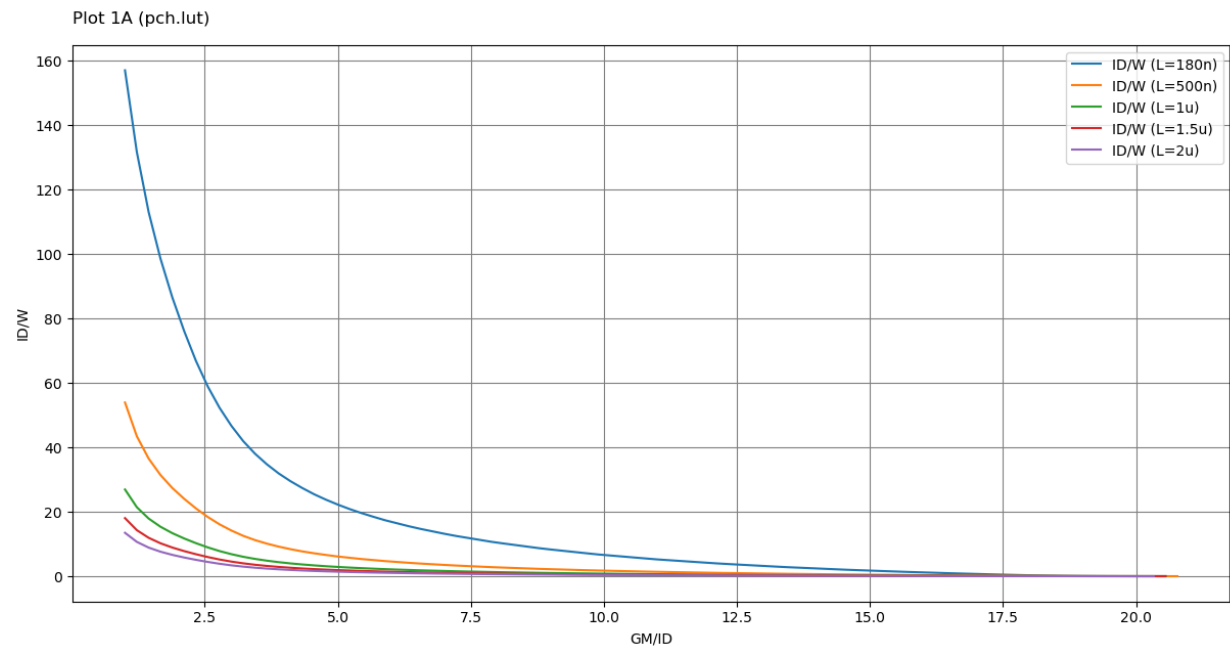


# gm/Cgg

## NMOS

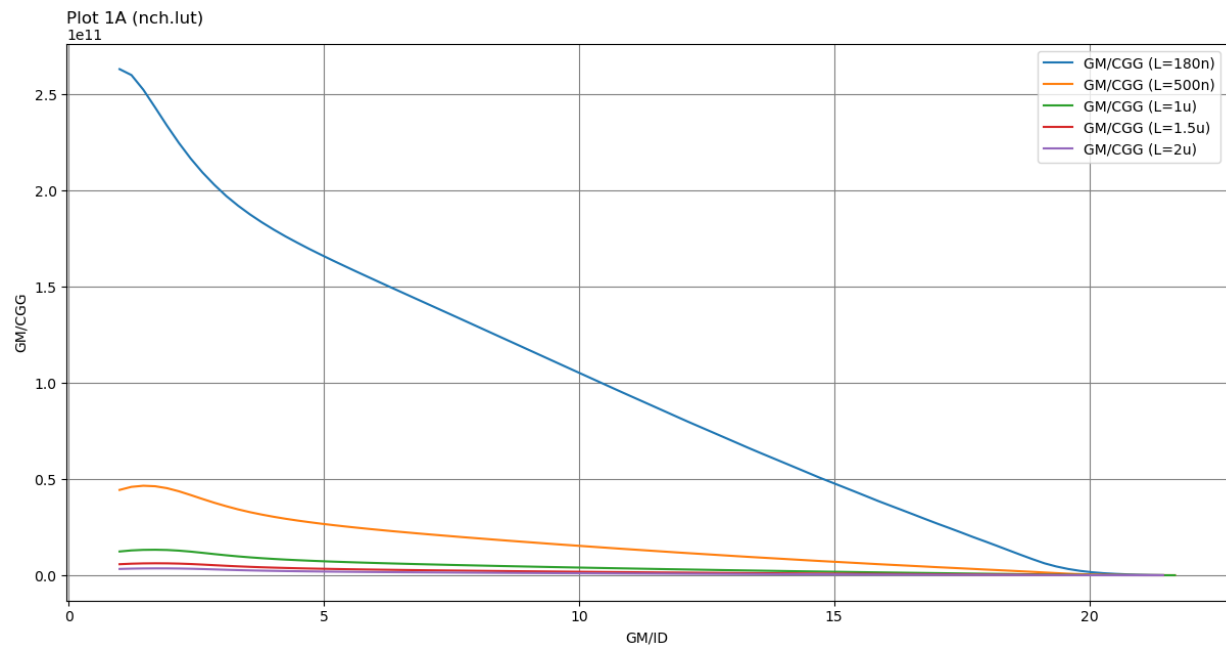


## PMOS

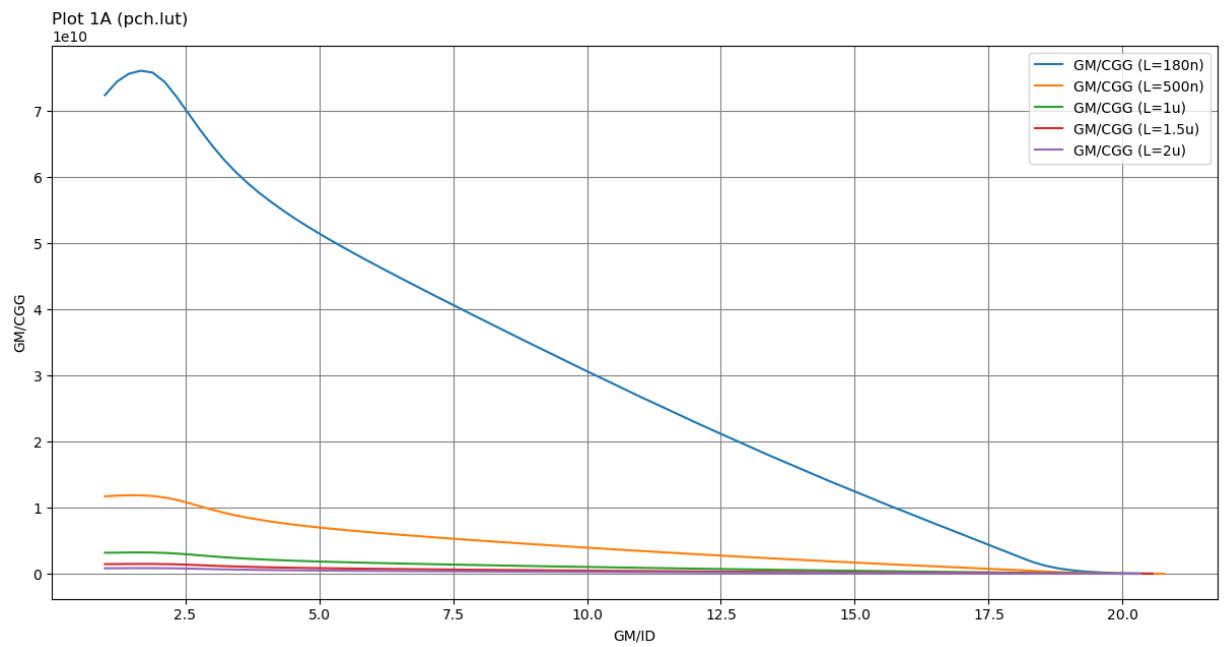


# VGS

## NMOS

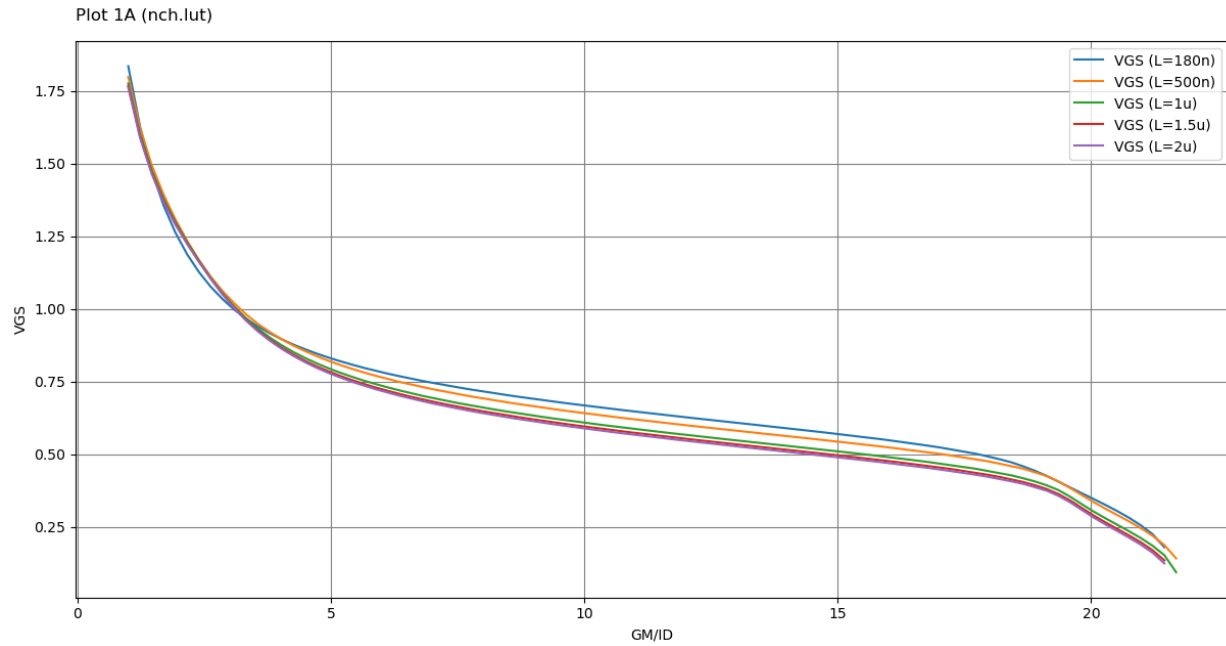

## PMOS

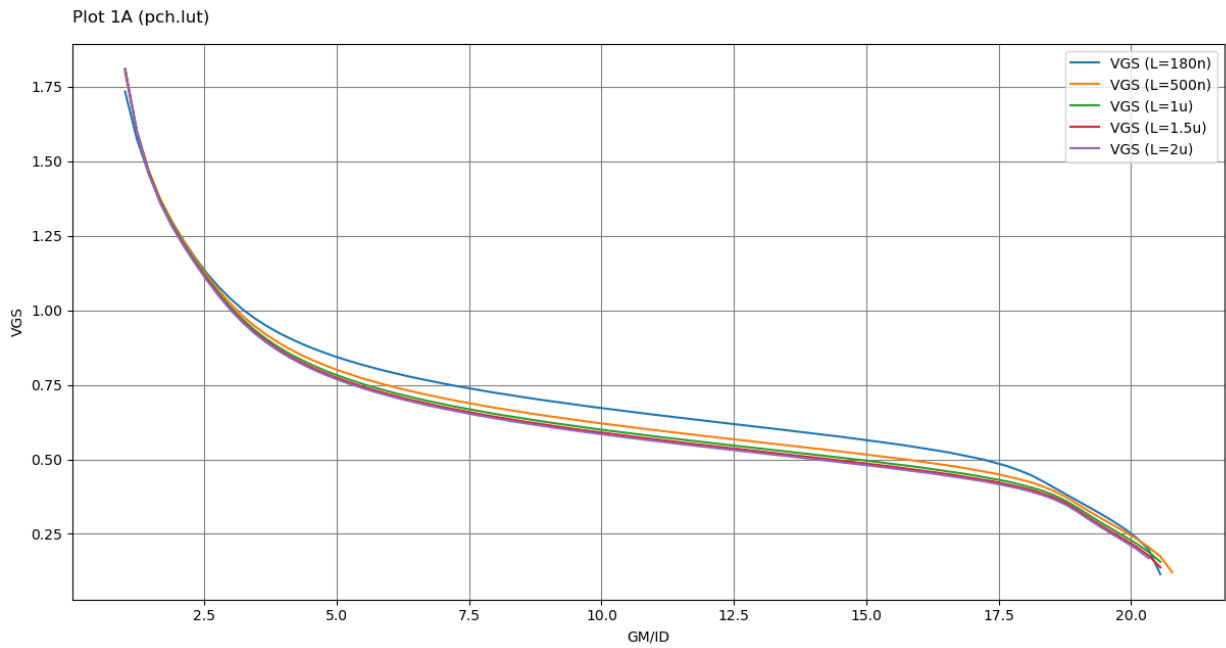

## PART 2: OTA Design

### General Hand Analysis

- Input pair should be PMOS because CMIR is closer to ground.
- $I_{SS} = 40\mu A$  for the input pair (CS), and  $40\mu A$  for the cascode branches (CG). The NMOS current sources in the bottom needs to sink  $80\mu A$  ( $2 \times 40\mu A$ )

### Differential PMOS Pair Sizing

- MI or WI & short L for optimum GBW and minimum capacitive loading.
- $I_D = 20\mu$  &  $g_m/I_D = 15$

$$L = 200n \text{ \& } W = 6.36\mu$$

### PMOS Tail Current Source Sizing

- SI & long L  $\rightarrow$  lower noise contribution
- $I_D = 40\mu$  and  $g_m/I_D = 10$

$$L = 1\mu \text{ \& } W = 34.66\mu$$

### NMOS CM Sizing

- SI & long L
- $I_D = 40\mu$  and  $g_m/I_D = 10$

$$L = 1\mu \text{ \& } W = 8.59\mu$$

| #  | Parameter | Value  |
|----|-----------|--------|
| 1  | ID        | 20u    |
| 2  | L         | 200n   |
| 3  | W         | 6.36u  |
| 4  | VGS       | 590.9m |
| 5  | VDS       | 600m   |
| 6  | VSB       | 0      |
| 7  | gm/ID     | 14.69  |
| 8  | Vstar     | 136.1m |
| 9  | ft        | 3.366G |
| 10 | gm/gds    | 32.65  |
| 11 | VA        | 2.223  |
| 12 | ID/W      | 3.145  |
| 13 | gm/W      | 46.2   |
| 14 | AREA      | 1.222n |

| #  | Parameter | Value  |
|----|-----------|--------|
| 1  | ID        | 40u    |
| 2  | L         | 1u     |
| 3  | W         | 34.66u |
| 4  | VGS       | 609.9m |
| 5  | VDS       | 600m   |
| 6  | VSB       | 0      |
| 7  | gm/ID     | 9.86   |
| 8  | Vstar     | 202.8m |
| 9  | ft        | 236.8M |
| 10 | gm/gds    | 120.1  |
| 11 | VA        | 12.18  |
| 12 | ID/W      | 1.154  |
| 13 | gm/W      | 11.38  |

| #  | Parameter | Value  |
|----|-----------|--------|
| 1  | ID        | 40u    |
| 2  | L         | 1u     |
| 3  | W         | 8.59u  |
| 4  | VGS       | 616m   |
| 5  | VDS       | 450m   |
| 6  | VSB       | 0      |
| 7  | gm/ID     | 9.856  |
| 8  | Vstar     | 202.9m |
| 9  | ft        | 960.6M |
| 10 | gm/gds    | 99.5   |
| 11 | VA        | 10.09  |
| 12 | ID/W      | 4.657  |
| 13 | gm/W      | 45.9   |

## PMOS CM Sizing

- SI & long L
- $ID = 20\mu$  and  $gm/ID = 10$

$$L = 1\mu \text{ \& } W = 17.47\mu$$

## PMOS Cascode Sizing


- MI or WI & moderate L
- $ID = 20\mu$  and  $gm/ID = 15$

$$L = 0.5\mu \text{ \& } W = 21.73\mu$$

## NMOS Cascode Sizing

- MI or WI & moderate L
- $ID = 20\mu$  and  $gm/ID = 15$


$$L = 0.5\mu \text{ \& } W = 5.31\mu$$

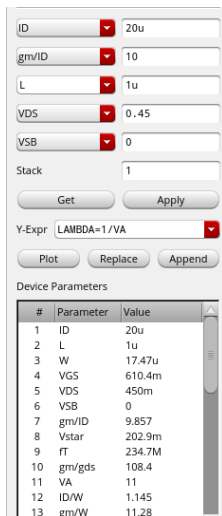

Y-Expr:  $LAMBDA=1/VA$

Device Parameters


| #  | Parameter | Value  |
|----|-----------|--------|
| 1  | ID        | 20u    |
| 2  | L         | 1u     |
| 3  | W         | 17.47u |
| 4  | VGS       | 610.4m |
| 5  | VDS       | 450m   |
| 6  | VS        | 0      |
| 7  | gm/ID     | 9.857  |
| 8  | Vstar     | 202.9m |
| 9  | IT        | 234.7M |
| 10 | gm/gds    | 108.4  |
| 11 | VA        | 11     |
| 12 | ID/W      | 1.145  |
| 13 | gm/W      | 11.28  |

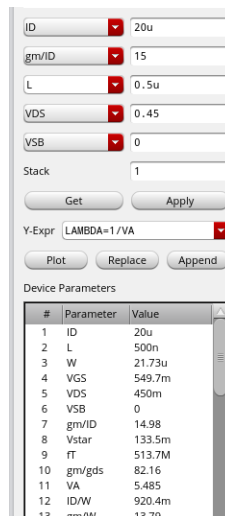

Y-Expr:  $LAMBDA=1/VA$

Device Parameters

| #  | Parameter | Value  |
|----|-----------|--------|
| 1  | ID        | 20u    |
| 2  | L         | 500n   |
| 3  | W         | 21.73u |
| 4  | VGS       | 549.7m |
| 5  | VDS       | 450m   |
| 6  | VS        | 0      |
| 7  | gm/ID     | 14.98  |
| 8  | Vstar     | 133.5m |
| 9  | IT        | 513.7M |
| 10 | gm/gds    | 82.16  |
| 11 | VA        | 5.485  |
| 12 | ID/W      | 920.4m |
| 13 | gm/W      | 13.79  |

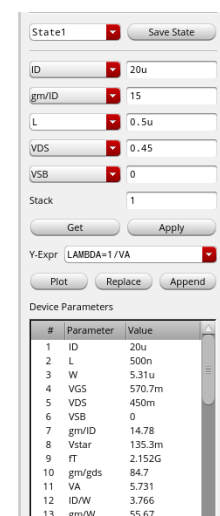

Y-Expr:  $LAMBDA=1/VA$




Device Parameters

| #  | Parameter | Value  |
|----|-----------|--------|
| 1  | ID        | 20u    |
| 2  | L         | 500n   |
| 3  | W         | 5.31u  |
| 4  | VGS       | 570.7m |
| 5  | VDS       | 450m   |
| 6  | VS        | 0      |
| 7  | gm/ID     | 14.78  |
| 8  | Vstar     | 135.3m |
| 9  | IT        | 2.152G |
| 10 | gm/gds    | 84.7   |
| 11 | VA        | 5.731  |
| 12 | ID/W      | 3.766  |
| 13 | gm/W      | 55.67  |

## VCASCN & VCASCP Selection

- $VCASCN \approx VGSN + V^* = 0.5707 + 0.2029 = 0.77$
- $VCASCP \approx VDD - |VGSP| - V^* = 1.8 - 0.5497 - 0.2029 = 1.05$
- Take margin for both (deeper in saturation)  $\rightarrow VCASCN = VCASCP = 0.9V$

**DC OP**

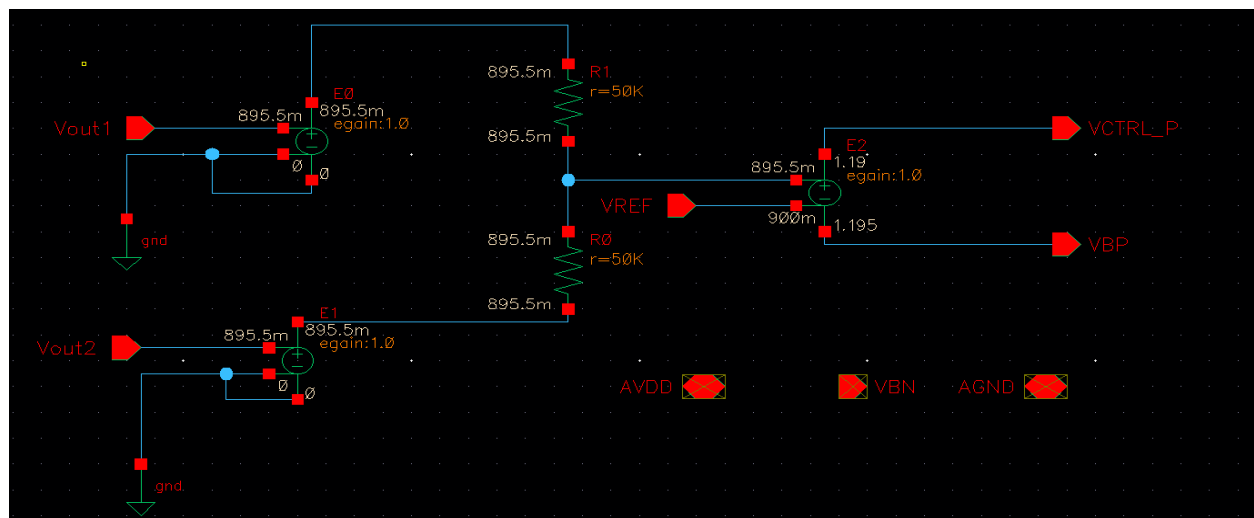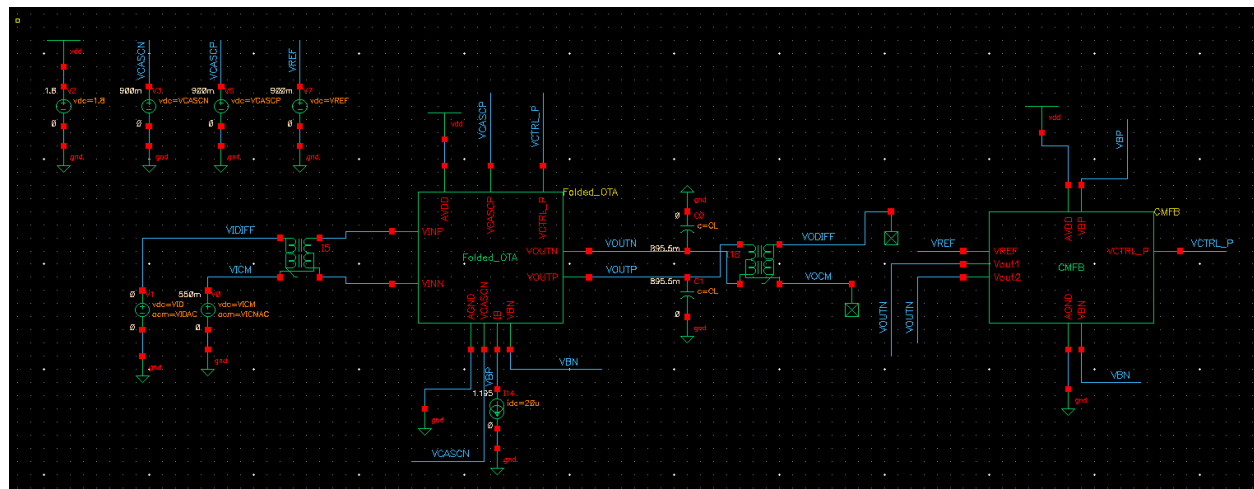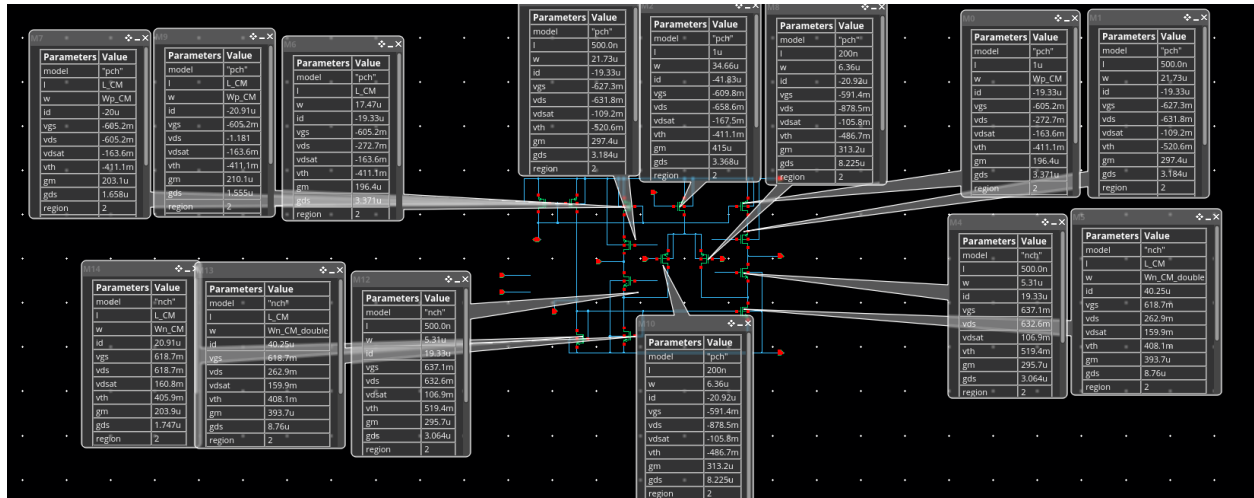

- $V_{out\_CM} = 895.5mV$
- The differential input (4.5m) = differential output voltage (4.5m). The relation is the error amplifier gain.

## Differential Small Signal

### Circuit Parameters


| Name  | Type | Details                                  | Value  |
|-------|------|--|--------|
| Ao    | expr | $y_{max}(mag(VF("/VODIFF")))$            | 1.86K  |
| Ao_dB | expr | $dB20(y_{max}(mag(VF("/VODIFF"))))$      | 65.39  |
| BW    | expr | $bandwidth(VF("/VODIFF"))$ 3 "low")      | 24.67K |
| UGF   | expr | $unityGainFreq(VF("/VODIFF"))$           | 46.47M |
| GBW   | expr | $(Ao * BW)$                              | 45.87M |
| PM    | expr | $phaseMargin(v("/VODIFF") ?result "ac")$ | 87.87  |

### Tuning:

- $ACL = \frac{AOL}{1+LG} \rightarrow AOL = 2(1 + 1000) = 2002$
- Increasing width of the input pair should increase the gain ( $W_{diff} = 10u$ ).

| Name  | Type | Details                                  | Value  |
|-------|------|--|--------|
| Ao    | expr | $y_{max}(mag(VF("/VODIFF")))$            | 2.011K |
| Ao_dB | expr | $dB20(y_{max}(mag(VF("/VODIFF"))))$      | 66.07  |
| BW    | expr | $bandwidth(VF("/VODIFF"))$ 3 "low")      | 25.86K |
| UGF   | expr | $unityGainFreq(VF("/VODIFF"))$           | 52.4M  |
| GBW   | expr | $(Ao * BW)$                              | 52.01M |
| PM    | expr | $phaseMargin(v("/VODIFF") ?result "ac")$ | 87.25  |

## Differential Gain vs Frequency

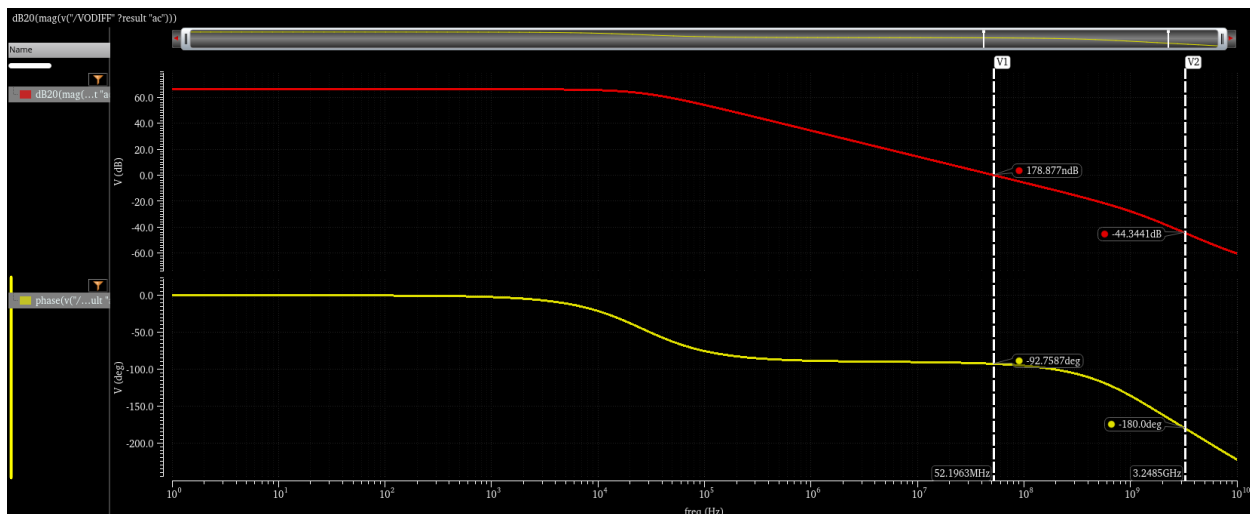



## Hand Analysis

- $R_{out} = [ro_{casc_n}(1 + (gm + gmb)(ro_{CM_n} || ro_{diff})) || [ro_{casc_p}(1 + (gm + gmb)ro_{CM_p})]]$
- $R_{out} = [326.4k(1 + (295.7 + 74)u * 55.56k)] || [314k(1 + (297.4 + 85.37)u * 296.7k)]$   
 $= 5.88M\Omega$
- $Av_{diff} = gm_{diff} * R_{out} = 355.6u * 5.88M = 2091.2 = 66.4dB$
- $f_p \approx \frac{1}{2\pi * R_{out} * CL} = \frac{1}{2\pi(5.88M)(1p)} = 27.1K$  (parasitic capacitances are neglected in this calculation)
- $GBW = UGF = Av * BW = 56.7 \text{ MHz}$
- $PM = 90 - \tan^{-1} \left( \frac{UGF}{\omega_{p_2}} \right) = 90 - \tan^{-1} \left( \frac{52.2M}{3.25G} \right) = 89.1 \text{ deg}$

|                  | Simulation | Hand Analysis |
|------------------|------------|---------------|
| <b>Av</b>        | 2011       | 2091          |
| <b>Av (dB)</b>   | 66.1       | 66.4          |
| <b>BW (KHz)</b>  | 25.86      | 27.1          |
| <b>GBW (MHz)</b> | 52.0       | 56.7          |
| <b>UGF (MHz)</b> | 52.4       | 56.7          |
| <b>PM (deg.)</b> | 87.25      | 89.1          |

## PART 4: Open-Loop OTA Simulation (Actual CMFB)

### Sizing

State1 Save State

ID 10u

gm/ID 10

L 1u

VDS 0.9

VSB 0

Stack 1

Get Apply

Y-Expr LAMBDA=1/VA

Plot Replace Append

Device Parameters

| #  | Parameter | Value  |
|----|-----------|--------|
| 1  | ID        | 10u    |
| 2  | L         | 1u     |
| 3  | W         | 8.56u  |
| 4  | VGS       | 608.7m |
| 5  | VDS       | 900m   |
| 6  | VSB       | 0      |
| 7  | gm/ID     | 9.869  |
| 8  | Vstar     | 202.7m |
| 9  | ft        | 239.8M |
| 10 | gm/gds    | 129.2  |
| 11 | VA        | 13.1   |
| 12 | ID/W      | 1.168  |

State1 Save State

ID 10u

gm/ID 15

L 1u

VDS 0.6

VSB 0

Stack 1

Get Apply

Y-Expr LAMBDA=1/VA

Plot Replace Append

Device Parameters

| #  | Parameter | Value  |
|----|-----------|--------|
| 1  | ID        | 10u    |
| 2  | L         | 1u     |
| 3  | W         | 5.61u  |
| 4  | VGS       | 536.8m |
| 5  | VDS       | 600m   |
| 6  | VSB       | 0      |
| 7  | gm/ID     | 14.65  |
| 8  | Vstar     | 136.5m |
| 9  | ft        | 565.9M |
| 10 | gm/gds    | 122.8  |
| 11 | VA        | 8.378  |
| 12 | ID/W      | 1.783  |

State1 Save State

ID 10u

gm/ID 10

L 1u

VDS 0.6

VSB 0

Stack 1

Get Apply

Y-Expr LAMBDA=1/VA

Plot Replace Append

Device Parameters

| #  | Parameter | Value  |
|----|-----------|--------|
| 1  | ID        | 10u    |
| 2  | L         | 1u     |
| 3  | W         | 2.14u  |
| 4  | VGS       | 615m   |
| 5  | VDS       | 600m   |
| 6  | VSB       | 0      |
| 7  | gm/ID     | 9.861  |
| 8  | Vstar     | 202.8m |
| 9  | ft        | 965.7M |
| 10 | gm/gds    | 113.9  |
| 11 | VA        | 11.55  |
| 12 | ID/W      | 4.673  |




- $V_{ref} = 1.23V$  &  $V_{CM} = 1.231V$
- $V_{OUTN} = V_{OUTP} = 709.mV$
- The differential input (1m) & differential output voltage (4m). The relation is the error amplifier gain.

## Differential Small Signal

### Circuit Parameters

| Name  | Type | Details                           | Value  |
|-------|------|-----------------------------------|--------|
| Av    | expr | $y_{max}(mag(VF"/VODIFF"))$       | 1.858K |
| Av_dB | expr | $dB20(y_{max}(mag(VF"/VODIFF")))$ | 65.38  |
| BW    | expr | $bandwidth(VF"/VODIFF")$ 3 "low"  | 27.09K |
| GBW   | expr | $(Av * BW)$                       | 50.32M |
| UGF   | expr | $unityGainFreq(VF"/VODIFF")$      | 50.25M |
| PM    | expr | $phaseMargin(VF"/VODIFF")$        | 87.28  |

### Differential Gain vs Frequency

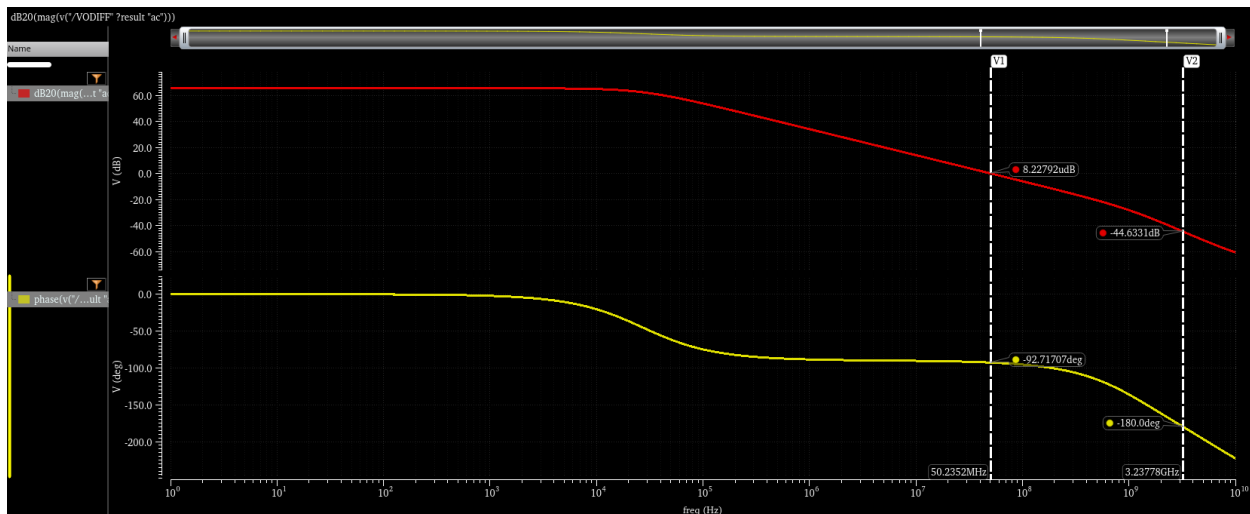

### Hand Analysis



- $R_{out} = [ro_{casc_n}(1 + (gm + gmb)(ro_{CM_n} || ro_{diff})) || [ro_{casc_p}(1 + (gm + gmb)ro_{CM_p})]]$
- $R_{out} = [296.3k(1 + (295.1 + 73.9)u * 55.1k)] || [322k(1 + (298.7 + 84.2)u * 300.7k)]$   
 $= 5.41M\Omega$
- $Av_{diff} = gm_{diff} * R_{out} = 355.4u * 5.41M = 1920 = 65.7dB$


- $f_p \approx \frac{1}{2\pi * R_{out} * C_L} = \frac{1}{2\pi(5.41M)(1p)} = 29.4K$  (parasitic capacitances are neglected in this calculation)
- $GBW = UGF = A_v * BW = 56.5 \text{ MHz}$
- $PM = 90 - \tan^{-1}\left(\frac{UGF}{\omega_{p_2}}\right) = 90 - \tan^{-1}\left(\frac{50.2M}{3.24G}\right) = 89.1 \text{ deg}$

|                  | Simulation | Hand Analysis |
|------------------|------------|---------------|
| <b>Av</b>        | 1858       | 1920          |
| <b>Av (dB)</b>   | 65.4       | 65.7          |
| <b>BW (KHz)</b>  | 27.1       | 29.4          |
| <b>GBW (MHz)</b> | 50.3       | 56.5          |
| <b>UGF (MHz)</b> | 50.3       | 56.5          |
| <b>PM (deg.)</b> | 87.3       | 89.1          |

## PART 5: Closed Loop Simulation (AC and STB Analysis)

**DC OP**

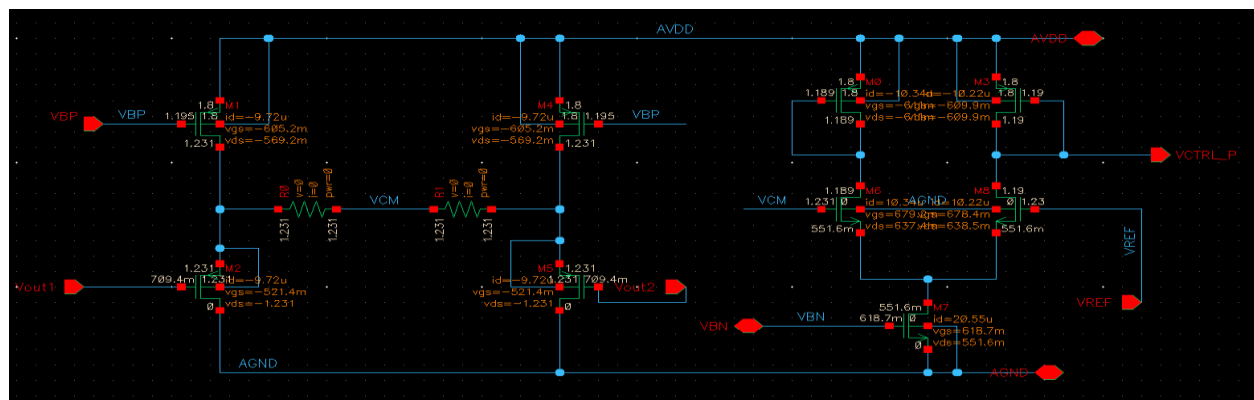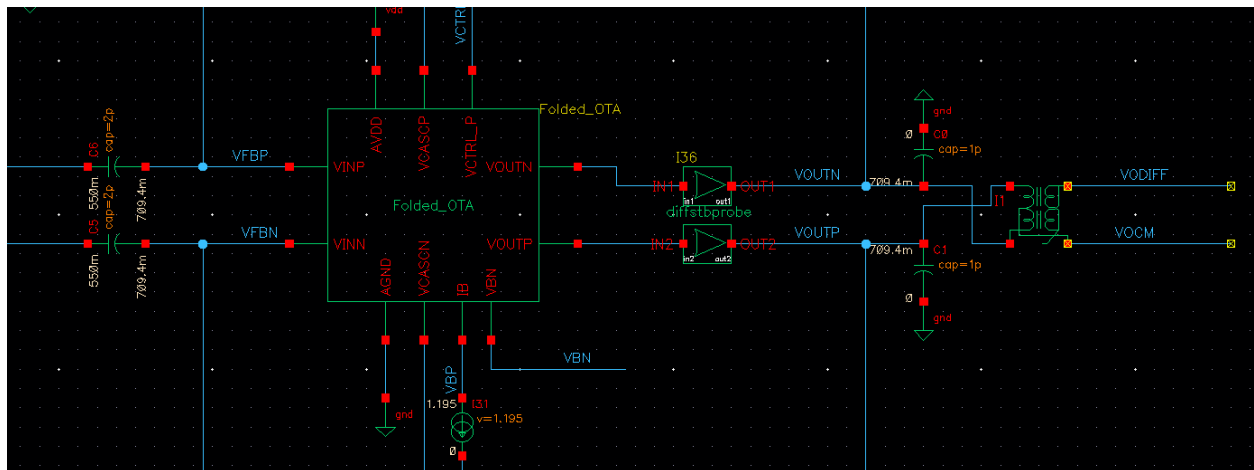

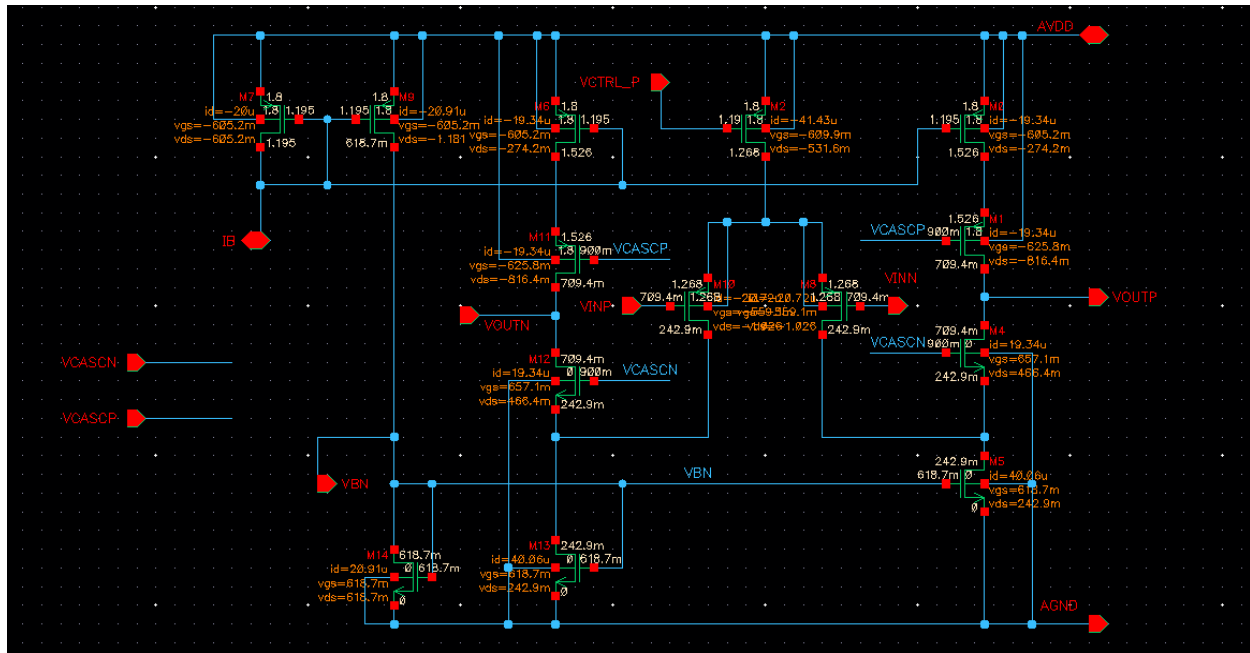

- $V_{out\_CM} = 709.4mV \rightarrow$  CMFB will reduce error till  $CM = V_{ref}$ .
- $V_{in\_CM} = 709.4mV \rightarrow$  due to feedback  $V_{out\_CM} = V_{in\_CM}$

## Differential Closed-Loop Response

| Name  | Type | Details  | Value  |
|-------|------|--|--------|
| Av    | expr | $y_{max}(mag(VF"/VODIFF"))$                    | 1.997  |
| Av_dB | expr | $dB20(y_{max}(mag(VF"/VODIFF")))$              | 6.007  |
| BW    | expr | $bandwidth(VF"/VODIFF") \cdot 3 \text{ "low"}$ | 10.9M  |
| GBW   | expr | $(Av \cdot BW)$                                | 21.77M |
| UGF   | expr | $unityGainFreq(VF"/VODIFF")$                   | 19.35M |
| PM    | expr | $phaseMargin(VF"/VODIFF")$                     | 96.14  |

## Differential & CMFB Loops Stability (STB analysis)


### Note

After the first run, we didn't meet the loop gain spec, so we multiply L & W of NMOS cascode transistor with factor of 4 ( $W=21.24\mu$  &  $L=4\mu$ ).


### AC Parameters

| Name  | Type | Details  | Value  |
|-------|------|--|--------|
| Av    | expr | $y_{max}(mag(VF"/VODIFF"))$                    | 1.999  |
| Av_dB | expr | $dB20(y_{max}(mag(VF"/VODIFF")))$              | 6.015  |
| BW    | expr | $bandwidth(VF"/VODIFF") \cdot 3 \text{ "low"}$ | 13.63M |
| GBW   | expr | $(Av \cdot BW)$                                | 27.25M |
| UGF   | expr | $unityGainFreq(VF"/VODIFF")$                   | 25.26M |
| PM    | expr | $phaseMargin(VF"/VODIFF")$                     | 70.03  |

## Magnitude (dB)

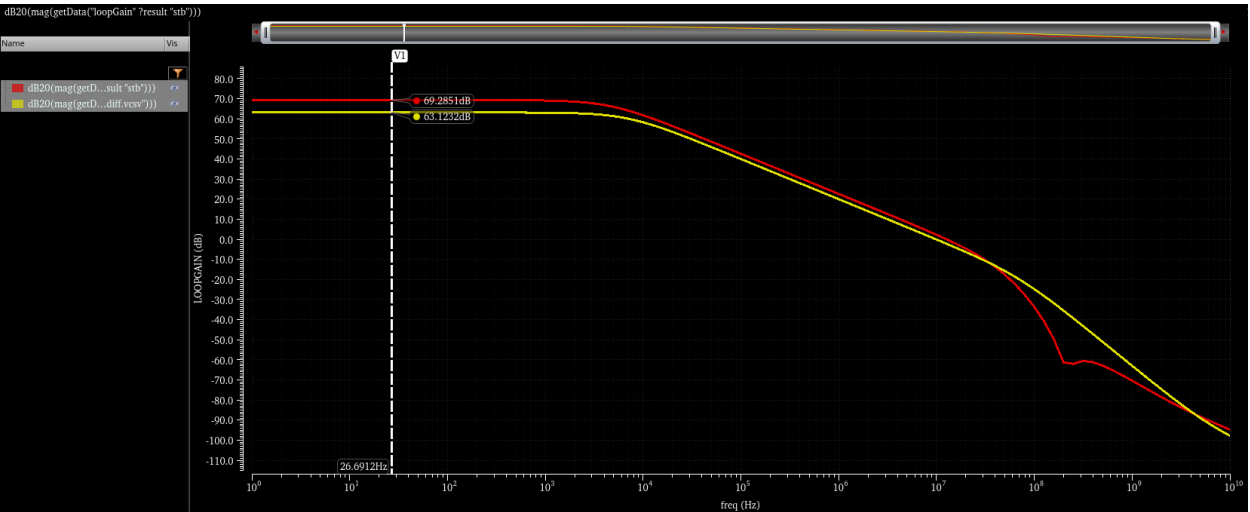

## Phase

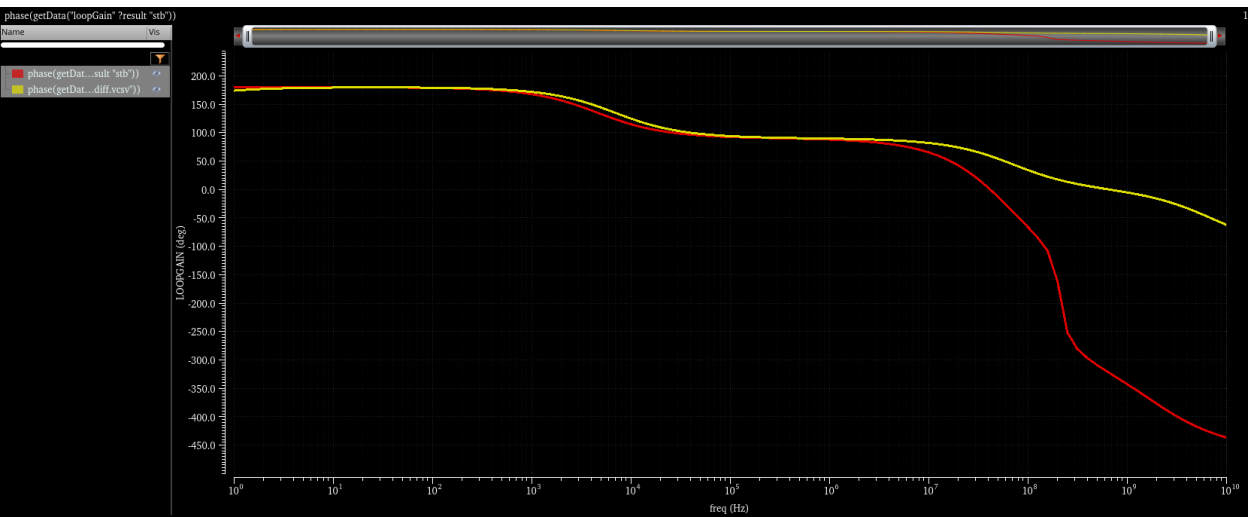

## Differential

| phaseMargin(getData("loopGain" ?result "stb")) |         |                   |       |
|--|---------|-------------------|-------|
| Expression                                     | Value   | Expression        | Value |
| 1 gainBwProd(get...                            | 9.899E6 | phaseMargin(ge... | 81.98 |

## Common

| gainBwProd(getData("loopGain" ?result "stb")) |         |                   |       |
|---|---------|-------------------|-------|
| Expression                                    | Value   | Expression        | Value |
| 1 gainBwProd(get...                           | 13.54E6 | phaseMargin(ge... | 59.04 |

## Comparisons

|           | Differential Loop | Common Loop |
|-----------|-------------------|-------------|
| GBW (MHz) | 9.90              | 13.5        |
| PM (deg.) | 82                | 59          |

**Comments:** Both differential and common loops are stable (PM > 45 deg). Differential loop meets the phase margin spec. Common loop has a relatively poor phase margin. Common loop GBW is higher than differential GBW.


|                | STB  | Open-Loop |
|----------------|------|-----------|
| GBW (MHz)      | 9.90 | 50.3      |
| Loop Gain (dB) | 63.1 | 66.2      |

**Comments:** Open-loop LG is higher than STB's LG because of the change in beta after adding the feedback capacitors. GBW is lower in closed loop due to decrease in gain.

## PART 6: Closed Loop Simulation (Transient Analysis)


### Differential & CMFB Loops Stability

#### Differential Input

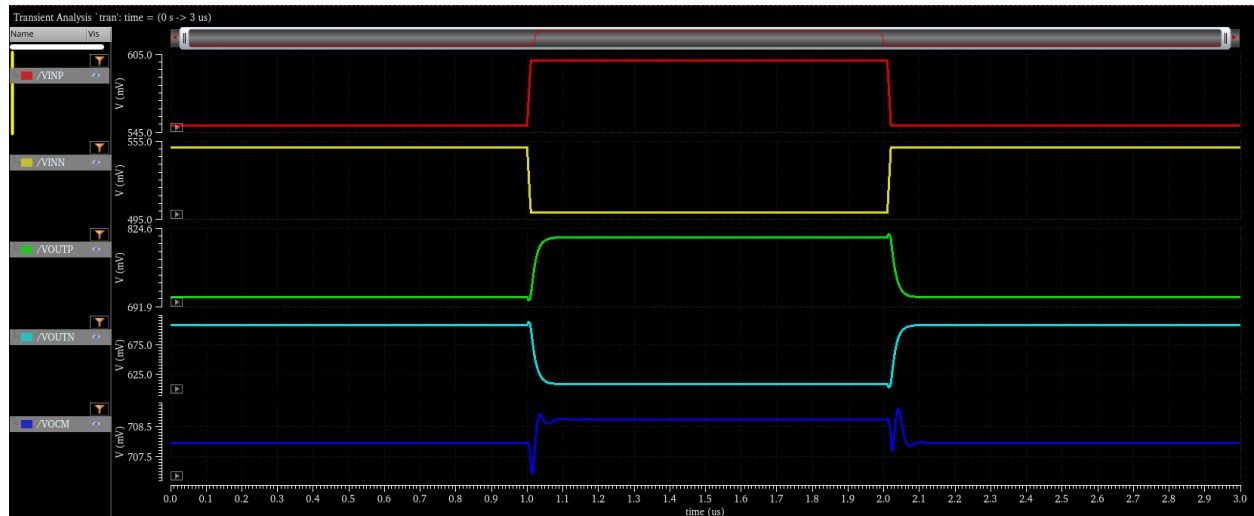

**Comment:** There is no ringing in differential loop, but there is ringing in the common loop. There is no spec on common loop PM, but increasing PM would reduce the ringing.


## Common Input

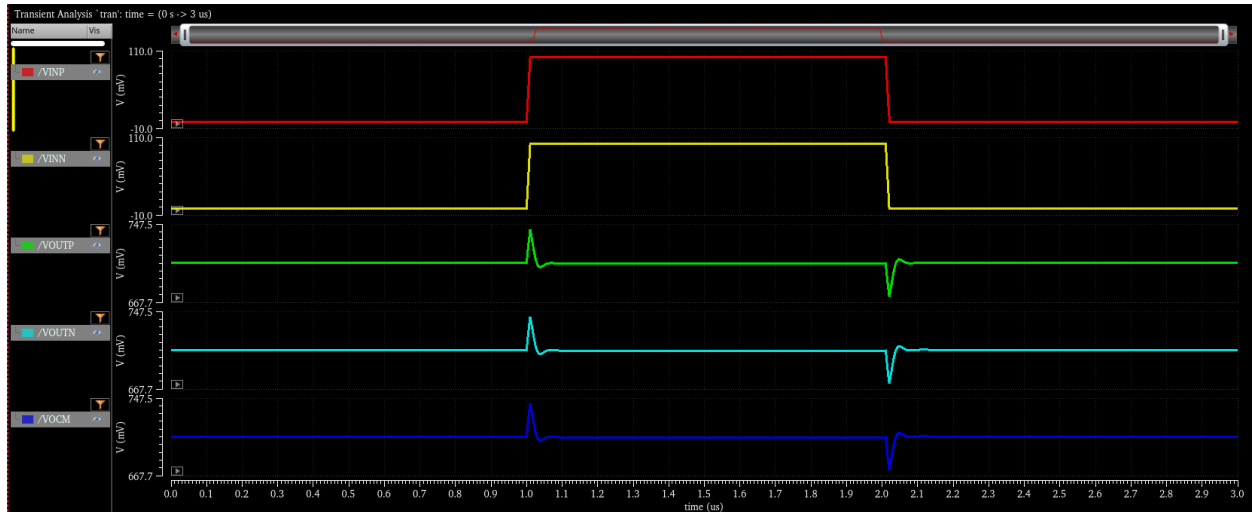

**Comment:** There is no ringing in differential loop, but there is small ringing in the common loop.


## Output Swing

VINP, VINN, VOUTP, VOUTN, and VOCM

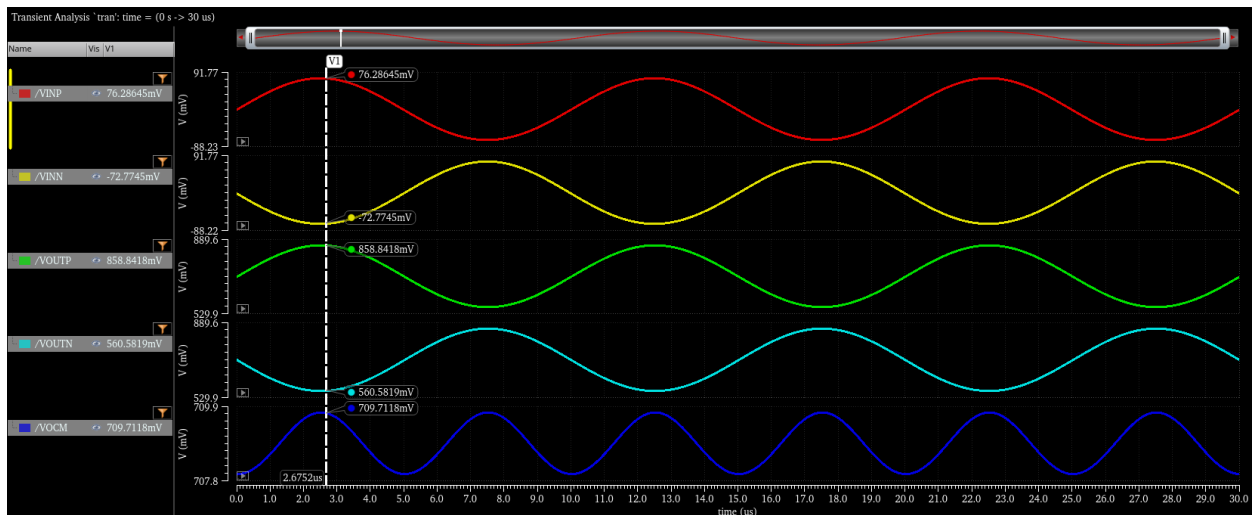




## VIDIFF and VODIFF

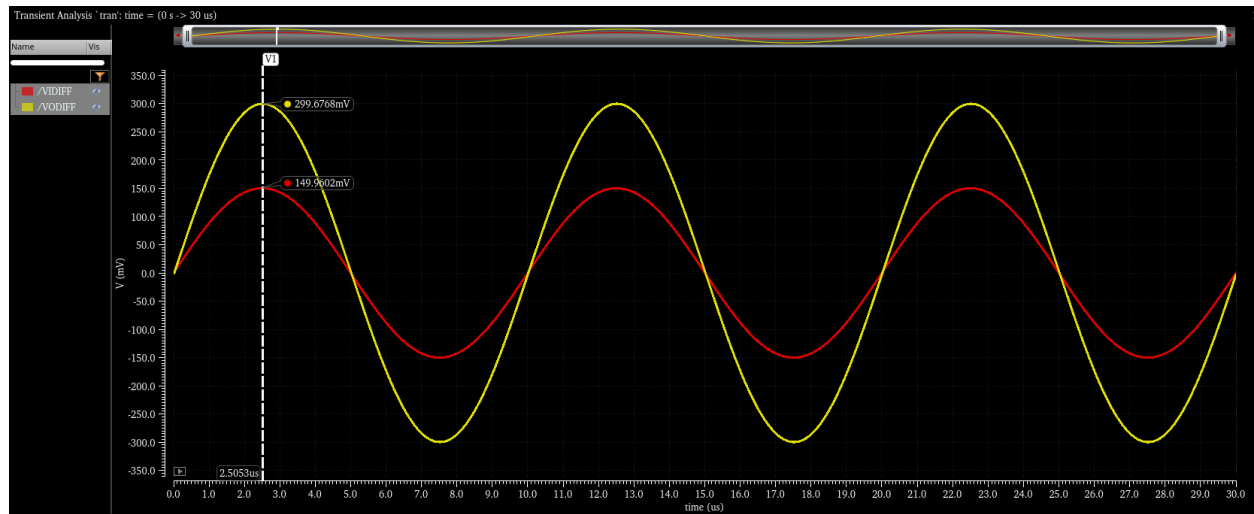

| Type | Details                   | Value  |
|------|---------------------------|--------|
| expr | peakToPeak(VT("/VIDIFF")) | 300m   |
| expr | peakToPeak(VT("/VODIFF")) | 599.5m |

|     |      |                          |       |
|-----|------|--------------------------|-------|
| ACL | expr | ymin(mag(VF("/VODIFF"))) | 1.999 |
|-----|------|--------------------------|-------|

## Spec Check

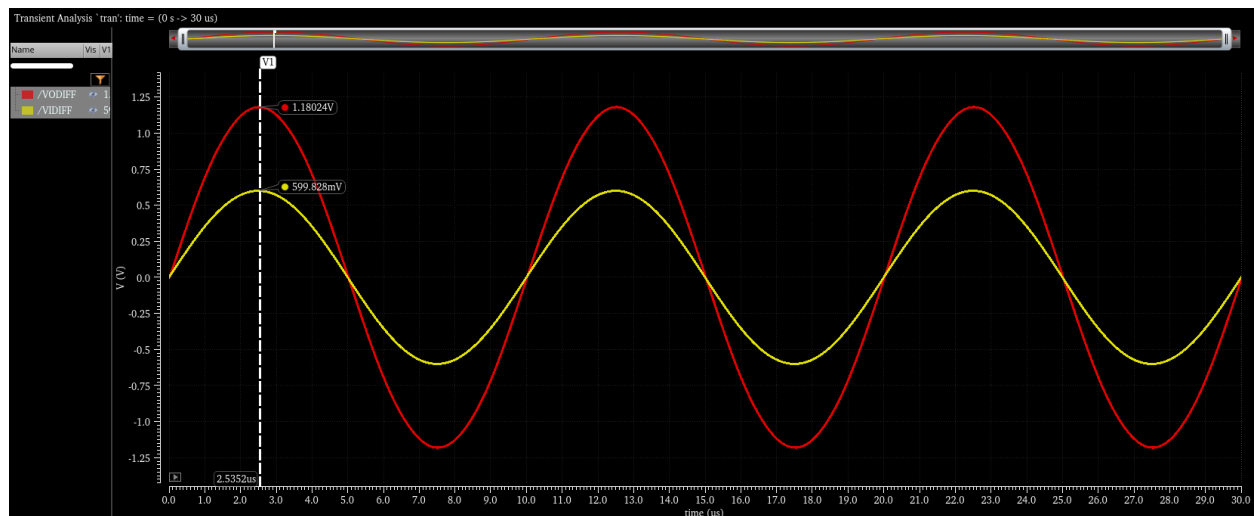

We can achieve more than 1.2pk-to-pk swing.

---

## Acknowledgments

As this is the final lab and project in the training, I would like to express my heartfelt gratitude to Dr. Hesham for his outstanding guidance and support throughout the past two months. He has been a great mentor and a source of inspiration for me. I also want to thank the teaching assistants, Eng. Roshan and Eng. Rawan, for their invaluable help in the labs. They have been very patient and helpful in debugging errors for everyone. Thank you for everything!